

November 29, 2024

## 1 MOSFET I-V characteristics

### 1.1 NMOS

$S$  at ground,  $D$  at  $V_{DD}$ .  $V_G \leq V_S$ , **cut-off** region.  $I_D = 0$ .  
 Otherwise, suppose  $V_G > V_S + V_{THN}$   
 If  $V_G \geq V_D + V_{THN}$ , in **linear (triode)** region.  
 If  $V_G < V_D + V_{THN}$ , in **saturation** region. Constant  $I_D$ .  
 NPN.  $V_G > V_S$  to draw electrons upwards to form bridge.

### 1.2 PMOS

$S$  at  $V_{DD}$ ,  $D$  at ground.  $V_G \geq V_S$ , **cut-off** region.  
 Otherwise, suppose  $V_G < V_S + V_{THP}$ ,  
 If  $V_G \leq V_D + V_{THP}$ , it is in **linear** region.  
 If  $V_G > V_D + V_{THP}$ , it is in **saturation** region.  
 To convert NMOS formulas to PMOS, substitute  $V_{GS}$  by  $V_{SG}$ ,  $V_{DS}$  by  $V_{SD}$ ,  $V_{THN}$  by  $V_{THP}$ .

### 1.3 Current Equations

In Linear region,  $I_D = k'_n \frac{W}{L} [(V_{GS} - V_{THN})V_{DS} - \frac{1}{2}V_{DS}^2]$   
 $I_D \approx k'_n \frac{W}{L} (V_{GS} - V_{THN})V_{DS}$ ;  $R_{DS} = \frac{1}{k'_n (W/L)(V_{GS} - V_{THN})}$   
 In Saturation region,  $V_{OD} = V_{GS} - V_{THN}$  (at least 200mV)

$$I_D = \frac{1}{2} k'_n \frac{W}{L} (V_{GS} - V_{THN})^2 (1 + \lambda V_{DS}) \quad \lambda \propto \frac{1}{L}$$

### 1.4 Small-Signal Model

#### 1.4.1 Simplified Model (In saturation)

$$i_d = g_m v_{gs}$$

$$g_m = \frac{\partial I_D}{\partial V_{GS}} = k'_n \frac{W}{L} (V_{GS} - V_{TH}) = \sqrt{2k'_n \frac{W}{L} I_D} = \frac{2I_D}{V_{GS} - V_{TH}}$$

#### 1.4.2 Output Resistance

Takes into account channel length modulation.

$$i_d = g_m v_{gs} + \frac{v_{ds}}{r_o}, \quad r_o = \frac{1}{\partial I_D / \partial V_{DS}} = \frac{1}{\lambda I_D}$$


### 1.4.3 Body Effect (bulk, source at diff voltage)

$$V_{THN} = V_{TH0} + \gamma \left[ \sqrt{|2\Phi_F - V_{BS}|} - \sqrt{|2\Phi_F|} \right]$$

$$\gamma = \frac{\sqrt{2q\epsilon_{si} N_{sub}}}{C_{ox}}, \quad \Phi_F = \pm \frac{kT}{q} \ln \frac{N_{sub}}{n_i} \quad (+ \text{NMOS}, - \text{PMOS})$$

$$g_{mb} = \frac{\partial I_D}{\partial V_{BS}} = g_m \frac{\gamma}{2\sqrt{|2\Phi_F - V_{BS}|}} = \eta g_m$$
 
$$i_d = g_m (v_{gs} + \eta v_{bs}) + \frac{v_{ds}}{r_o}$$



## 2 Common Source Amplifier

- $V_{swing} = 2 \times \min(V_{sw}^+, V_{sw}^-)$
- With resistive load,  $A_v = -g_m R_D$  ( $R_D \ll r_o$ ).  $V_{out} = V_{DD} - I_D R_D$ , so increasing gain by increasing  $R_D$  results in reduced  $V_{swing}$ .
- Current source has high AC resistance but low DC resistance.  $A_v = -g_{m1}(r_{o1} \parallel r_{o2})$

### 2.1 Buffer


 


Figure 1: Two port amplifier, with buffer (right)

- (L)  $A_{ov} = \frac{r_i}{r_i + R_S} A_v \frac{R_L}{r_o + R_L}$ , so small  $r_i$  or  $R_L$  reduces gain.  
 (R)  $A_{ov} = A_v \frac{r_{ib}}{r_{ib} + r_o} A_{vb} \frac{R_L}{R_L + r_{ob}}$ , ideal buffer has  $r_{ib} = \infty$  and  $r_{ob} = 0$ , source follower has those characteristics.

### 2.2 Source Follower

 

$$A_v = \frac{g_{m1}}{g_{m1} + g_{mb1} + \frac{1}{r_{o1}} + \frac{1}{r_{o2}}}$$

$$\approx \frac{g_{m1}}{g_{m1} + g_{mb1}}$$


$$= \frac{1}{1 + \eta}$$

$$r_{out} = (r_{s1} \parallel r_{o2})$$

$$= \left( \frac{1}{(1 + \eta)g_{m1}} \parallel r_{o2} \right)$$


$$\approx \frac{1}{(1 + \eta)g_{m1}}$$

## 2.3 Common Gate Amplifier

 

$$A_v \approx (g_{m1} + g_{mb1})(r_{o1} \parallel r_{o2})$$

## 2.4 Cascode Amplifier

 

$$A_v = -g_{m1}g_{m3}r_{o4}r_{o3}/2$$

$$A_v = -g_{m1}r_{o3}$$


$$r_{out} = (g_{m2} + g_{mb2})r_{o1}r_{o2}$$

about twice the gain of CS amplifier

$$\parallel g_{m3}r_{o3}r_{o4}$$

Max. swing is  $V_{DD} - 4V_{OD}$

## 2.5 Equivalent Resistance Patterns

 

$$(L) \quad r_{eq} = [1 + (g_{m1} + g_{mb1})R_s]r_{o1}$$


$$(R) \quad r_{eq} \approx \frac{1}{g_{m1} + g_{mb1}}$$

$r_{eq}$  through a reverse diode connection is  $\frac{1}{g_m}$
 
## 3 Frequency Response


- Poles correspond to capacitors shunting to ground (low-pass filters). Multiply by input impedance, at  $f = \frac{1}{2\pi RC}$
- Zeros correspond to capacitors across inverting amplifiers, creating destructive interference.
- For capacitance along signal path across amplifier with non-zero input resistance, it also behaves as a miller cap, becoming a capacitor shunting to ground at the amplifier input but with a capacitance multiplied by the gain.
- Miller theorem misses a zero by removing the feedforward path

- If lowest pole is separated from other poles by at least 4x, then that pole is the dominant pole, and 3dB frequency can be estimated as that pole
- Associate poles with nodes, zeros with feedforward paths across capacitors, for CS amplifier, poles are  $\frac{1}{RC}$ , zero is in the right half plane at  $\frac{gm}{C_{GD}}$


 
## 4 Current Sources

- Transistor in saturation behaves like a current source
- Simple current source is to use resistor divider to set  $V_G$  to put transistor in saturation - not good because PVT (process, voltage, temperature) variation affects  $V_{GS}$  and  $I_D$  is related to  $V_{GS}^2$



Current Mirror  
 $\frac{I_{out}}{I_{in}} = \frac{W_2/L_2}{W_1/L_1}$

- Current mirror is less affected by PVT since only depends on single resistor
- Current mirror is like a I-to-V-to-I converter
- $V_{out} \geq V_{GS} - V_{TH} = V_{OD}$  so minimum  $V_{out}$  is 1 over-drive voltage
- Gain Error (Systematic Error)

$$E_{rr} = \frac{I_{out} - I_{out,ideal}}{I_{out,ideal}} = \frac{\lambda(V_{out} - V_{in})}{1 + \lambda V_{in}} \approx \lambda(V_{out} - V_{in})$$

- Mismatch Error (Random Error) can be reduced by using same W & L but multiple fingers to "vary" W

### 4.1 Cascode Current Mirror

 


Figure 2: Cascode Current Mirror v1, v2, v3, final

Cascode current mirrors eliminate systematic gain error by matching  $V_{in}$  and  $V_{out}$

- (1)  $r_{out} = (1 + g_{m3}r_{o2})r_{o3}$
- (2)  $V_{omin} = V_{th} + 2V_{OD}$
- (3)  $V_{omin} = 2V_{OD}$ ,  $r_{out} \approx g_{m3}r_{o2}r_{o3}$
- (4) To generate  $V_B$  for (3)

## 5 Differential Amplifier

- Differential input:  $v_{id} = v_{i1} - v_{i2}$
- Differential output:  $v_{od} = v_{o2} - v_{o1}$
- Common-mode input:  $v_{ic} = (v_{i1} + v_{i2})/2$
- Common-mode output:  $v_{oc} = (v_{o2} + v_{o1})/2$

Single-ended gain:

$$A_{v1} = -\frac{1}{2}g_{m1}(r_{o1}/R_D); A_{v2} = \frac{1}{2}g_{m2}(r_{o2}/R_D)$$

Differential gain:  $A_{vd} = g_{m1}(r_{o1}/R_D)$

Maximum differential input voltage is input range such that after amplifying, output range is within the swing.

### 5.1 Offset Voltage

Output offset voltage is the output when  $v_{id} = 0$ .


Input offset voltage is the input  $v_{id}$  to make output offset voltage equal to 0.

### 5.2 Common-mode Gain

$$A_{cm} = \frac{v_{o2} - v_{o1}}{v_{ic}}$$

For single-ended matched current source load,
 
$$A_{cm,s} = \frac{-g_{m2}/g_{m3}}{1 + 2g_{m2}r_{o5}}$$



### Common-mode Rejection Ratio (CMRR)

$$CMRR(dB) = 20 \log\left(\frac{A_{vd}}{A_{cm}}\right)$$

## 6 Operational Amplifiers

Two stage op amp typically for voltage output

Cascode op amp typically for current output because of high output impedance

Two stage op amp is differential pair cascaded with cs amplifier

systematic offset is assuming no difference between differential inputs, then distance of output away from half vdd

## 7 Frequency Response (2)

Barkhausen Criteria for amplifier instability

Gain condition  $|A(\omega)\beta(\omega)| = 1$

Phase condition  $\angle A(\omega)\beta(\omega) = -180^\circ$

Gain margin is 0 dB - gain when phase shift is  $-180^\circ$

Phase margin is phase when gain is 1 -  $(-180^\circ)$

### 7.1 Compensation Capacitor

Moves the lower pole lower and the high pole higher, by increasing  $C_{gd5}$ .

But it also moves the zero closer to the imaginary axis, introducing more lagging phase shift.

### 7.2 Lead Compensation


Add resistor  $R_c$  and capacitor  $C_c$  across amplifying transistor.

Effect is  $\omega_z = \frac{1}{C_c(\frac{1}{g_{m5}} - R_c)}$ , originally  $\frac{g_{m5}}{C_{gd5}}$

Choose  $\omega_z$  slightly higher than  $\omega_u$ , the unity gain bandwidth, e.g.  $1.2\omega_u$

If  $R_c > \frac{1}{g_{m5}}$  the zero moves to LHP.

## 8 Bias Circuits

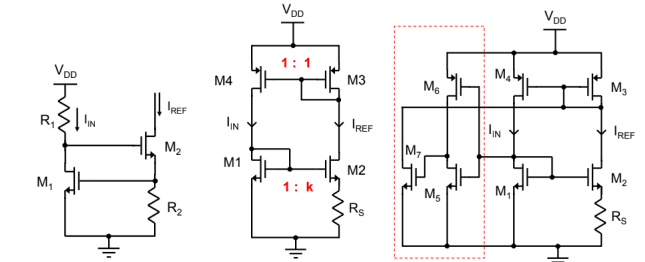


(L) Threshold referenced  $I_{REF} = \frac{V_{THN} + \sqrt{2 \frac{I_{IN}}{k'_n} \frac{W_1}{L_1}}}{R_2}$

 (C) Self-biasing current source  $I_{REF} \approx \frac{2}{k'_n \frac{W_1}{L_1} R_S^2} \left(1 - \frac{1}{\sqrt{k}}\right)^2$

$g_{m1} = \sqrt{2k'_n \frac{W_1}{L_1} I_{D1}} = \frac{2}{R_S} \left(1 - \frac{1}{\sqrt{k}}\right)$  (indp. of  $V_{DD}$  and  $V_{th}$ )

(R) Start up circuit, when current is 0,  $M_5$  is off and  $M_6$  is on. when circuit is started,  $M_5$  is on and  $M_6$  is off



$$V_{OD1} = V_{QD5}$$

$$g_{m5} = \frac{W_5/L_5}{W_1/L_1} g_{m1} \text{ is constant}$$